 


# Lecture 2

## 4CS015: Digital

### Electronics



Prepared by: Uttam Acharya

# 1. Coverage

## 1.1. Boolean Logic and Logic Gates

### 1.1.1. Truth Table

## 1.2. Boolean Algebra Laws

## 1.3. Combinational Circuit

# 1.1.A Boolean Logic

George Boole (1815-1864)

- “An Investigation into the Laws of Thought”
- Defined an algebra for solving logical problems
- Limited to dealing with facts True or False
- Now known as Boolean Algebra

# Basic Logic Definitions

- In a Logic System a variable can have one of two possible states.
- Single capital letters are used to represent variables.
- The bits 1 and 0 are also used as constants.

<b>TRUE</b>	<b>ON</b>	<b>CLOSED</b>	<b>'1'</b>	<b>Yes</b>	<b>5v</b>
<b>FALSE</b>	<b>OFF</b>	<b>OPEN</b>	<b>'0'</b>	<b>No</b>	<b>1v</b>

## 1.1 Boolean Logic & Logic Gates

### 1.1.A Boolean Logic

## 1.1.B Logic States

- If a switch is closed:
  - The light will be ON.
  - This can represent Logic TRUE.
- If a switch is open:
  - The light will be OFF.
  - This can represent Logic FALSE.
- The switch is a Logic variable.

### 1.1 Boolean Logic & Logic Gates

#### 1.1.A Boolean Logic

# 1.1.B.a Boolean Basics: Operators

- Boole defined three basic operations that could be used with these Boolean variables.

- AND

- OR

- NOT

- All logical expressions can be built from these three.

## 1.1 Boolean Logic & Logic Gates

### 1.1.A Boolean Logic

### 1.1.B Logic States

# 1.1.B.a Boolean Basics: Operators


## 1.1 Boolean Logic & Logic Gates

### 1.1.A Boolean Logic


### 1.1.B Logic States

### a.Boolean Operators


- Logical **AND**

 

- Logical **OR**

 


- Logical **NOT**

 

# 1.1.B.a.a Logical AND

- How can we switch the light on?

 

1.1 Boolean Logic & Logic Gates

1.1.A Boolean Logic

1.1.B Logic States

a.Boolean Operators




## 1.1.B.a.a Logical AND

- Boolean Expression:

$$F = A \quad \text{AND} \quad B \quad \text{or} \quad F = A \cdot B$$

- Gate Diagram:

 

- Truth Table:

Input A	Input B	Output F
0	0	0
0	1	0
1	0	0
1	1	1

# 1.1.B.a.a AND Relationship

- Boolean representation . **(Period)**
- If F,A and B are Boolean variables.
- Then the expression  $F = A \cdot B$  means
  - F is only true when A AND B are both true.
- As A is capable of being 1 or 0 and B is capable of being 1 or 0 there are 4 possible states. 00, 01, 10 or 11

Input A	Input B	Output F
0	0	0
0	1	0
1	0	0
1	1	1

## 1.1.B.a.b Logical OR


- How can we switch on the light?

### 1.1 Boolean Logic & Logic Gates

#### 1.1.A Boolean Logic

#### 1.1.B Logic States

#### a.Boolean Operators

 


## 1.1.B.a.b Logical OR

- Boolean Expression:

$$F = A \text{ OR } B \text{ alternatively } F = A + B$$

- Gate Diagram:

 

- Truth Table:

Input A	Input B	Output F
0	0	0
0	1	1
1	0	1
1	1	1



## 1.1.B.a.b OR Relationship

- Boolean representation + **(Plus)**
- If F,A and B are Boolean variables.
- Then the expression  $F = A+B$  means
  - F is only true when A OR B, OR both, are true.
- As A is capable of being 1 or 0 and B is capable of being 1 or 0 there are 4 possible states. 00, 01, 10 or 11

Input A	Input B	Output F
0	0	0
0	1	1
1	0	1
1	1	1
  
# 1.1.B.a.c Logical Not

- How can we switch the light off?
- Boolean Expression:
- **$F = \text{NOT } A$**  or  $F = !A$  or  $F = \bar{A}$
- Gate Diagram:
- Truth Table:



Input A	Output F
0	1
1	0

# 1.1.B.a.c Boolean Not

- The NOT relationship reverses the value.
- NOT True is False etc...
- The Symbol( $\neg$ ) used is usually a bar above the variable or expression to be reversed
- E.g if  $A = \text{true}$  then  $\bar{A} = \text{false}$
- In some circumstances we use !
- E.g. if  $B = \text{true}$   $!B = \text{false}$  (easier to type)

## 1.1 Boolean Logic & Logic Gates

### 1.1.A Boolean Logic

### 1.1.B Logic States

### a.Boolean Operators


### a.c Logical Not

# 1.1.B Integrated Circuit and Logic Gates

## 1.1 Boolean Logic & Logic Gates

### 1.1.A Boolean Logic

### 1.1.B Logic States

 



## 1.1.B Other Logic Gates

### 1.1 Boolean Logic & Logic Gates

#### 1.1.A Boolean Logic

#### 1.1.B Logic States

- To make life a little easier the basic logical functions are expanded to include:
  - **NAND**
    - This is an AND with a NOT output.
  - **NOR**
    - This is an OR with a NOT output.
  - **XOR**
    - This is the Exclusive OR function.
  - **XNOR**
    - This is Complement of XOR.

## 1.1.B NAND

- Boolean Expression:

$$F = \text{NOT}(A \text{ AND } B) \quad \text{or} \quad \overline{F} = \overline{A \cdot B}$$

- Gate Diagram:



- Truth Table:

Input A	Input B	Output F
0	0	1
0	1	1
1	0	1
1	1	0

### 1.1 Boolean Logic & Logic Gates

#### 1.1.A Boolean Logic


#### 1.1.B Logic States

## 1.1.B NOR

- Boolean Expression:

$$F = \text{NOT}(A \text{ OR } B) \text{ or } \overline{F} = \overline{A+B}$$

- Gate Diagram:

 

- Truth Table:

Input A	Input B	Output F
0	0	1
0	1	0
1	0	0
1	1	0

1.1 Boolean Logic & Logic Gates

1.1.A Boolean Logic


1.1.B Logic States

## 1.1.B XOR

- Boolean Expression:

$$\mathbf{F = A \text{ XOR } B \text{ or } F = A \oplus B}$$

- Gate Diagram:

 

- Truth Table:

Input A	Input B	Output F
0	0	0
0	1	1
1	0	1
1	1	0

### 1.1 Boolean Logic & Logic Gates

#### 1.1.A Boolean Logic


#### 1.1.B Logic States

## 1.1.B XNOR

- Boolean Expression:

$$F = A \text{ XNOR } B \text{ or } F = A \odot B$$

- Gate Diagram:

 

- Truth Table:

Input A	Input B	Output F
0	0	1
0	1	0
1	0	0
1	1	1

### 1.1 Boolean Logic & Logic Gates

#### 1.1.A Boolean Logic

#### 1.1.B Logic States

## 1.2 Boolean Algebra Laws

The operations  $+$ ,  $\cdot$  And  $'$  consequently satisfy the basic laws 1, 2 and 3 of Boolean algebra. That is:

$$A + B \equiv B + A$$

$$A \cdot B \equiv B \cdot A$$

Commutative Laws

$$(A + B) + C \equiv A + (B + C)$$

$$(A \cdot B) \cdot C \equiv A \cdot (B \cdot C)$$

Associative Laws

$$A \cdot (B + C) \equiv (A \cdot B) + (A \cdot C)$$

$$A + (B \cdot C) \equiv (A + B) \cdot (A + C)$$

Distributive Laws

1.1 Boolean Logic & Logic Gates

1.2 Boolean Algebra Laws



## 1.2 Boolean Algebra Laws

### Identity Law

$$A + 0 = A$$

$$A \cdot 1 = A$$

### Negation Law

low = high

$$(0 = 1)$$

### Idempotent Law

$$A + A = A$$

$$A \cdot A = A$$

### Double Negation Law

$$\overline{\overline{A}} = A$$

### Complement Law

$$A \cdot A = 0$$

$$A + A = 1$$

### Domination Law

$$A + \text{high} = \text{high}$$

$$(A + 1 = 1)$$

$$A \cdot \text{low} = \text{low}$$

$$A \cdot 0 = 0$$

### Absorption Law

$$A + (A \cdot B) = A$$

$$A \cdot (A + B) = A$$

1.1 Boolean Logic & Logic Gates


1.2 Boolean Algebra Laws

# 1.2 DeMorgan's Laws

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$

## 1.1 Boolean Logic & Logic Gates

### 1.2 Boolean Algebra Laws

 

A	B	A+B	$\overline{A+B}$	$\bar{A}$	$\bar{B}$	$\bar{A} \cdot \bar{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0



## 1.1 Boolean Logic & Logic Gates

### 1.2 Boolean Algebra Laws

**Question 1 : NAND and NOR gates are called universal gates, why?**

## 1.1 Boolean Logic & Logic Gates

### 1.2 Boolean Algebra Laws

## 1.2.a Precedence of operators

- As with normal mathematics when working out the value of a function it is very important to do it in the right order.
- NOT AND OR
- Parenthesis (brackets) override in the normal way.
- When a bar goes above more than 1 symbol it becomes a bracket that reverses.

# 1.2 Example

## 1.1 Boolean Logic & Logic Gates

### 1.2 Boolean Algebra Laws

#### a. Precedence of operators

Where

A=1

B=1

C=0


D=1

E=0

G=1

Evaluate  
these

examples

 

Example 1.  $F = A.B.C$

Example 2.  $F = C.A.B$

Example 3.  $F = \overline{A} + B + C$

Example 4.  $F = A.B + C$

Example 5.  $F = A + B.C$


Example 6.  $F = \overline{A + B}.C$

Example 7.  $F = A .B + (C + A) .D + E + G$

## 1.3 Circuit Design

1.1 Boolean Logic & Logic Gates

1.3 Circuit Design

 


## 1.3 Digital Component

### 1.1 Boolean Logic & Logic Gates

#### 1.3 Circuit Design

- The main thing to remember is that combinations of gates implement Boolean functions.
- The circuit below implements the Boolean function:

$$F(X, Y, Z) = X + \bar{Y}Z$$

 

**We simplify our Boolean expressions so that we can create simpler circuits.**

## 1.3.a Digital Component

### 1.1 Boolean Logic & Logic Gates

#### 1.3 Circuit Design

#### 1.3.a Digital Component

- We have designed a circuit that implements the Boolean function:  $F(X, Y, Z) = X + \bar{Y}Z$
- This circuit is an example of a *combinational logic* circuit.
- **Combinational logic** circuits produce a specified output (almost) at the instant when input values are applied.
  - In a later section, we will explore circuits where this is not the case.

## 1.3.b Truth Table

### 1.1 Boolean Logic & Logic Gates

#### 1.3 Circuit Design

#### 1.3.a Digital Component

$$F(x, y, z) = x\bar{z} + y$$


x	y	z	$\bar{z}$	$x\bar{z}$	$x\bar{z} + y$
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	0	0	1

# 1.3.c Simple Combinational Circuit

## Example

$$\begin{aligned} F &= \overline{A.B} + A.B + B.C \\ &= \overline{A.(B+B)} + B.C \\ &= A.1 + B.C \\ &= A + B.C \end{aligned}$$

### Circuit after Simplification

 

1.1 Boolean Logic & Logic Gates

1.3 Circuit Design

1.3.a Digital Component



## 1.3.c Simple Combinational Circuit

### Example

$$F = \overline{A}.B.C + A.\overline{B}.C + A.B.\overline{C} + A.B.C$$

$$= \overline{A}.B.C + A.\overline{B}.C + A.B.\overline{C} + A.B.C + A.B.C + A.B.C$$

$$= (\overline{A}.B.C + A.B.C) + (A.\overline{B}.C + A.B.C) + (A.B.\overline{C} + A.B.C)$$

$$= (\overline{A} + A).B.C + (\overline{B} + B).C.A + (\overline{C} + C).A.B$$

$$= B.C + C.A + A.B$$

1.1 Boolean Logic & Logic Gates

1.3 Circuit Design

1.3.a Digital Component



# 1.3.c Simple Combinational Circuit

## Example

**Simplify:**

$$\mathbf{X = (A.B.C) + (A.B'.C) + (A'.B.C)}$$

1.1 Boolean Logic & Logic Gates

1.3 Circuit Design

1.3.a Digital Component



## 1.3.d Exercises

**Simplify and construct the logic circuit:**

$$1. A'.B' + (A.B)'$$

$$2. (A + B).(A + B) + A.(A + B')$$

$$3. (A.B'.C' + A'.B'.C + A.B.C + A'.B.C')$$

1.1 Boolean Logic & Logic Gates

1.3 Circuit Design

1.3.a Digital Component

# Summary

- We have looked at the basic logic gates:
  - Identifying OR, AND, NOT, NAND, NOR and XOR.
- We have seen that gates can be joined together to form Combinatorial Logic.

# Thank you